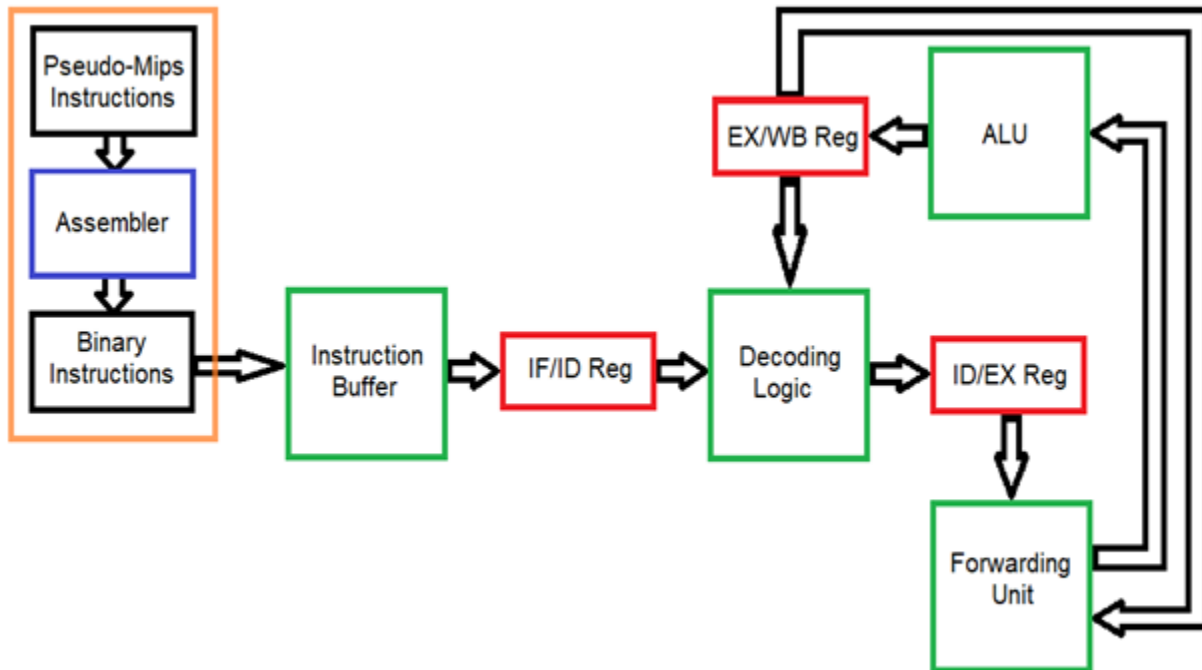


Goals

The purpose of this project was to implement a structural and behavioral design of a four-stage pipelined multimedia unit with a reduced set of multimedia instructions. The pipeline is similar to those in the Sony Cell SPU and Intel SSE architectures. The pipeline was developed in a structural/RTL manner with several modules operating simultaneously. Each module represents a pipelined stage with its interstage register. The components incorporated were an ALU, control unit, forwarding unit, instruction buffer and various intermediate registers. These components fit together in a pipeline, that is a chain of tasks that allow for multiple instructions to be worked on in an assembly line fashion. These instructions have been written and coded in a pseudo-mips manner so that the pipeline and its components can operate in unison. The instructions are read in the instruction buffer, and passed through to the ALU, where they are logically executed. The forwarding unit is able to catch and assist with hazards that certain instructions may bring up. All throughout are interstate registers, that allow for the system to “pulse” on a clock signal, allowing for each stage to be executed and then have its data passed on to the next. The end results are able to be compared to our expected results, generated by the testbench. When all of the components are brought together under the Pipeline toplevel, we are able to see the flow of data through each cycle of execution and how the various registers are manipulated along the way.

Block Diagram

The overall function of the multimedia unit can be expressed through the following diagram:



Key: External (Assembler), Register, Pipeline Unit

Following the diagram, we convert pseudo-mips instructions into 25-bit binary instructions in the assembler. These instructions then pass to the instruction buffer, where they are primed in the pipeline. Passing through the IF/ID register, they reach the decoding logic, where the instruction type and necessary register names are retrieved. Next in the line is the forwarding unit, which is capable of retrieving data that has already been calculated for use and also sends the necessary information to the ALU for calculation. After calculations are made, the final data is stored in the EX/WB register, and made available to the pipeline again by inserting it back into the loop.

Design Procedure

The objective was to create a more efficient multimedia unit design than the single cycle processor. This pipeline needs just the clock signal to start the process. The interstate registers are designed to carry data between modules in the datapath. Each is clocked so that multiple instructions can be carried out at once without altering the datapath modules. The only data needed to be passed throughout the pipeline is the 25-bit instruction code, registers, and control bits. Interstate Registers dissect the instruction to give the datapath all the information needed to execute, but doesn't pass unnecessary data.

Functionality

ALU

The ALU takes up to three inputs from the register file and calculates the result based on the current instruction to be performed. As seen below by the port declarations you can see rs1,rs2 and rs3 as the three inputs from the register file.

```
entity ALU is
  port(
    rs1 : in std_logic_vector(127 downto 0);
    rs2 : in std_logic_vector(127 downto 0);
    rs3 : in std_logic_vector(127 downto 0);
    loadIndex : in std_logic_vector(2 downto 0);
    immediate : in std_logic_vector(15 downto 0);
    alu_out : out std_logic_vector(127 downto 0);
    control : in std_logic_vector(4 downto 0)
  );
end ALU;
```

When control has a value of 00000 we load a 16-bit immediate value from the instruction field into a 16 bit field specified by the Load Index. This can be seen below where the value for immediate is determined by the Load Index.

```
--Load Immediate
when "00000" =>
  alu_out <= x"00000000000000000000000000000000";
  case loadIndex is
    when "111" => --7
      alu_out(127 downto 112) <= immediate;
    when "110" => --6
      alu_out(111 downto 96) <= immediate;
    when "101" => --5
      alu_out(95 downto 80) <= immediate;
    when "100" => --4
      alu_out(79 downto 64) <= immediate;
    when "011" => --3
      alu_out(63 downto 48) <= immediate;
    when "010" => --2
      alu_out(47 downto 32) <= immediate;
    when "001" => --1
      alu_out(31 downto 16) <= immediate;
    when others => --0
      alu_out(15 downto 0) <= immediate;
  end case;
```

Signal name	Value	
rs1_tb	0	0
rs2_tb	0	0
rs3_tb	0	0
loadIndex_tb	111	111 110 101 100 011 010 001
immediate_tb	0003	0003
alu_out_tb	15576890575...	55340232221128654848 844424930131968 12884901888 196608
control_tb	00000	00000

Here we verify the Load Immediate where we load a 16-bit Immediate value (0000000000000011) into rd from index 63 downto 48

Signal name	Value	240
alu_out_tb[63]	0	
alu_out_tb[62]	0	
alu_out_tb[61]	0	
alu_out_tb[60]	0	
alu_out_tb[59]	0	
alu_out_tb[58]	0	
alu_out_tb[57]	0	
alu_out_tb[56]	0	
alu_out_tb[55]	0	
alu_out_tb[54]	0	
alu_out_tb[53]	0	
alu_out_tb[52]	0	
alu_out_tb[51]	0	
alu_out_tb[50]	0	
alu_out_tb[49]	1	
alu_out_tb[48]	1	
alu_out_tb[47]	0	

The instruction to be performed is dependent on the value given by the input control. The inputs from the register file are used to calculate the result which is outputted to alu_out. Here we verify the instruction Signed Integer Multiply-Add Low with Saturation when control has a value of 00001. We multiply rs3 and rs2, then add the products to rs1 and output the result. The values can be verified by checking the decimal values, for rs1 = 3, rs2 = 4, rs3 = 8. The output for this operation should be 35 and this is verified by the waveform.

```
--Signed Integer Multiply-Add Low with Saturation
when "00001" =>
  for i in 0 to 3 loop
    offset := 32*i;
    var16_1:= rs3((15 + offset) downto (0 + offset));
    var16_2 := rs2((15 + offset) downto (0 + offset));
    var32_1 := rs1((31 + offset) downto (0 + offset));
    var32_2 := std_logic_vector((signed(var16_1) * signed(var16_2)));
    var32_3 := std_logic_vector(signed(var32_1) + signed(var32_2));

    if ((var32_1(31) = '0') and (var32_2(31) = '0') and (var32_3(31) /= '0')) then
      alu_out((31 + offset) downto (0 + offset)) <= X"7FFFFFFF";
    elsif ((var32_1(31) = '1') and (var32_2(31) = '1') and (var32_3(31) /= '1')) then
      alu_out((31 + offset) downto (0 + offset)) <= X"80000000";
    else
      alu_out((31 + offset) downto (0 + offset)) <= var32_3;
    end if;
  end loop;
```

Signal name	Value	400	440	480	520	560	600
rs1_tb	0	0					3
rs2_tb	0	0					4
rs3_tb	0	0					8
loadIndex_tb	7						
immediate_tb	0003	0003					C0C9
alu_out_tb	15576890575...	3	35	3	4294967267	3	
control_tb	00000	00000	00001	00010	00011	00100	

Here we verify the instruction XOR when control has a value of 11000. The result is calculated by taking the XOR of rs1 and rs2. The values can be verified by checking the decimal values, for rs1 = 1, rs2 = 2. The output for this operation should be 3 and this is verified by the waveform.

Signal name	Value	1880	1920	1960
<input checked="" type="checkbox"/> <code>rs1_tb</code>	0	1		
<input checked="" type="checkbox"/> <code>rs2_tb</code>	0	2		
<input checked="" type="checkbox"/> <code>rs3_tb</code>	0	3		
<input checked="" type="checkbox"/> <code>loadIndex_tb</code>	011	000		
<input checked="" type="checkbox"/> <code>immediate_tb</code>	0003	80FC		
<input checked="" type="checkbox"/> <code>alu_out_tb</code>	84442493013...	3		
<input checked="" type="checkbox"/> <code>control_tb</code>	00000	11000		


Register File

The register file has 32 128-bit registers. On any cycle, there can be 3 reads and 1 write which is denoted by signals rd_reg1, rd_reg2, rd_reg3 and wr_reg respectively. When executing instructions, each cycle two/three 128 bit- register values are read. One 128-bit result can be written if the write signal is valid. The implementation is shown below with signal write_En determining when it can be written.

```
begin

rs3 <= data when write_En = '1' and wr_reg = rd_reg3 else registers(to_integer(unsigned(rd_reg3)));
rs2 <= data when write_En = '1' and wr_reg = rd_reg2 else registers(to_integer(unsigned(rd_reg2)));
rs1 <= data when write_En = '1' and wr_reg = rd_reg1 else registers(to_integer(unsigned(rd_reg1)));

process (clk)
begin
    if (rising_edge(clk)) then
        if write_En = '1' then
            case index is
                when "0111" => --7
                    registers(to_integer(unsigned(wr_reg)))(127 downto 112) <= data(127 downto 112);
                when "0110" => --6
                    registers(to_integer(unsigned(wr_reg)))(111 downto 96) <= data(111 downto 96);
                when "0101" => --5
                    registers(to_integer(unsigned(wr_reg)))(79 downto 64) <= data(79 downto 64);
                when "0100" => --4
                    registers(to_integer(unsigned(wr_reg)))(79 downto 64) <= data(79 downto 64);
                when "0011" => --3
                    registers(to_integer(unsigned(wr_reg)))(47 downto 32) <= data(47 downto 32);
                when "0010" => --2
                    registers(to_integer(unsigned(wr_reg)))(47 downto 32) <= data(47 downto 32);
                when "0001" => --1
                    registers(to_integer(unsigned(wr_reg)))(31 downto 16) <= data(31 downto 16);
                when "0000" => --0
                    registers(to_integer(unsigned(wr_reg)))(15 downto 0) <= data(15 downto 0);
                when others => --full
                    registers(to_integer(unsigned(wr_reg))) <= data;
            end case;
        end if;
    end if;
end if;
```

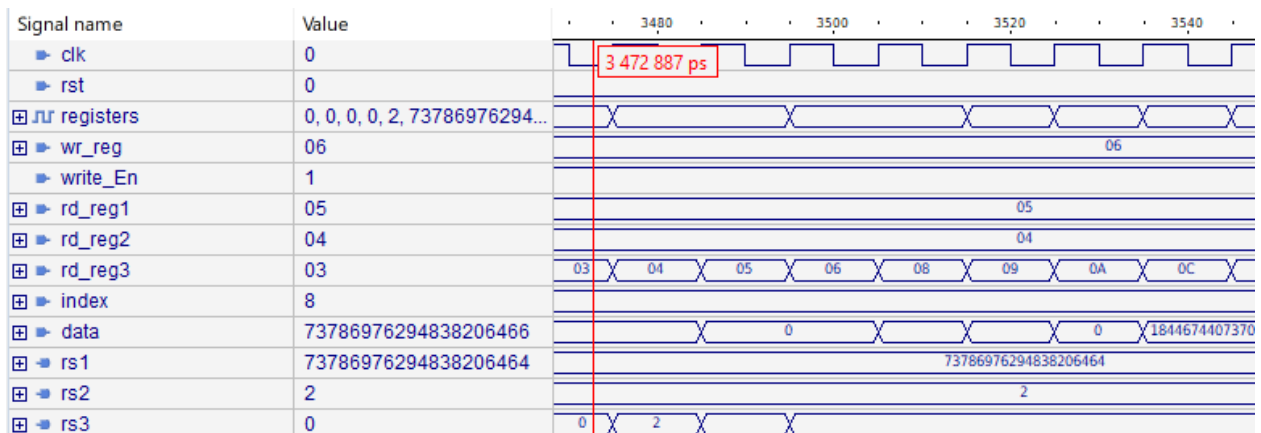

As seen, the Register File correctly reads the register numbers inputted and outputs the values of the selected registers in the next clock cycle when write_En is 1. The values given at rd_reg1, rd_reg2, and rd_reg3 indicate the index for the array registers on which register to read. Based on that index it displays the registers corresponding to it for rs1, rs2 and rs3 respectively. Signal wr_reg here is used to determine which register is being written and corresponds to the index in the registers array. Signal data corresponds to the register number corresponding to that index.

Instruction Buffer

The instruction buffer can store 64 25-bit instructions. As seen below we have an input for the 25 bit instruction. We have an array that can store all 64 instructions into array arr.

```
entity InstBuffer is
port(
    clk : in std_logic;

    wr_en : in std_logic;
    inst_in : in std_logic_vector(24 downto 0);

    addr : in std_logic_vector(5 downto 0);
    inst_out : out std_logic_vector(24 downto 0)
);
end InstBuffer;

architecture behavioral of InstBuffer is
type arr is array (0 to 63) of bit_vector(24 downto 0);
signal buff : arr;
signal PC : integer := 0;
begin
```

On each cycle, the instruction specified by the Program Counter (PC) is fetched, and the value of PC is incremented by 1. As seen below, the instruction is fetched on the rising edge of the clock and when write enabled is 1. After the instruction is fetched, the PC is reset back to 0 if all the instructions have been fetched otherwise it is incremented by 1.


```


begin
  process(clk)
  begin
    if rising_edge(clk) then
      if(wr_en = '1') then
        buff(PC) <= to_bitvector(inst_in);

        if(PC = 63) then
          PC <= 0;
        else
          PC <= PC + 1;
        end if;
      end if;
    end if;
  end process;

  inst_out <= to_stdlogicvector(buff(to_integer(unsigned(addr))));
end behavioral;

```

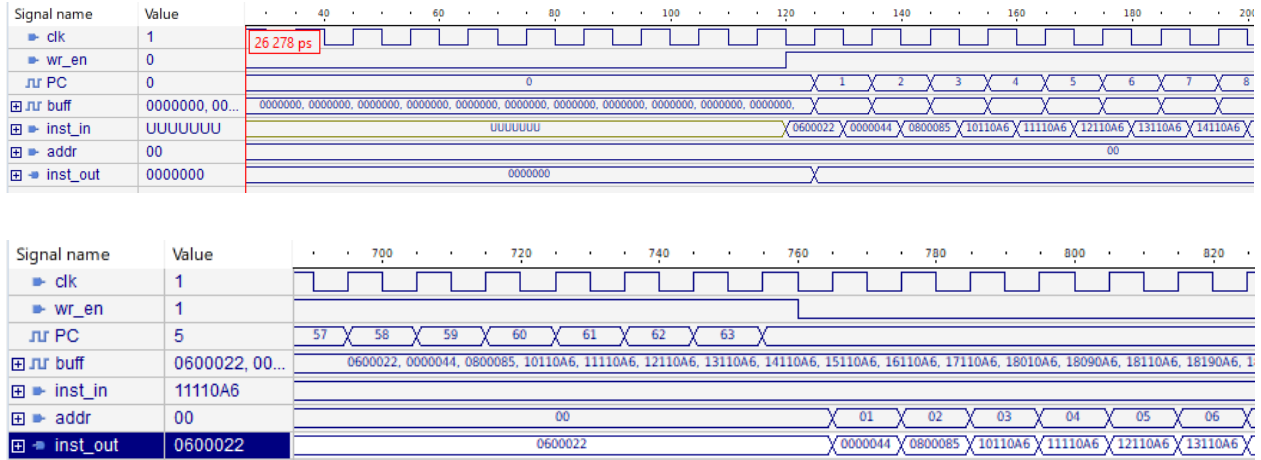The operation of the instruction buffer can be verified below, where the instruction fetched is specified by the increment program counter. Once the program counter is reset to 0, we are able to notice at inst_out the instruction output increments with our addr signal and matches those instruction fetched by the program counter.



Forwarding Unit


Every instruction uses the most recent value of a register. The forwarding unit ensures that only valid data and source/destinations registers are being considered for forwarding. As shown below, data is forwarded when signal write enable, $rf_we,1 = 1$ and when the most recent data to be forwarded matches the data from one of the inputs from the register. When both conditions are met, the data will be forwarded and can be represented with a value of one corresponding to which register value was forwarded.

```
architecture Behavioral of DataForwarding is
begin
process (rf_we, rf_wr_reg, rs1_reg, rs2_reg, rs3_reg)
begin
    if (rf_we = '1' and rf_wr_reg = rs1_reg) then
        fw1 <= '1';
    else
        fw1 <= '0';
    end if;

    if (rf_we = '1' and rf_wr_reg = rs2_reg) then
        fw2 <= '1';
    else
        fw2 <= '0';
    end if;

    if (rf_we = '1' and rf_wr_reg = rs3_reg) then
        fw3 <= '1';
    else
        fw3 <= '0';
    end if;
end process;
end architecture;
```

 As shown below, we have $rf_we = 1$ and the most recent data having a value of 5. The value matching that comes from register 1 and results in it being forwarded which is indicated by $fw1$ having a value of 1 and $fw2$ and $fw3$ having a value of 0, indicating it is not forwarded.



Four- Stage Pipeline

The pipeline is implemented as a structural model with modules for each corresponding pipeline stages and their interstage registers. Four instructions can be at different stages of the pipeline at every cycle and all instructions take four cycles to complete. Clock edge-sensitive pipeline registers separate the If, ID, EXE, and WB stages. Data is written to the register file after the WB stage.

Stage 1

```
--Stage 1: Instruction Fetch
ProgramCounter: reg generic map (DWIDTH => 6)
port map (
    CLK => CLK,
    RST => RESET,
    CE  => run,
    D   => adder_out,
    Q   => pc_out
);

PCadder: adder generic map (DWIDTH => 6)
port map (
    A => "000001",
    B => pc_out,
    D => adder_out
);

InstBuffer_inst: InstBuffer
port map (
    clk => CLK,

    wr_en => wr_en,
    inst_in => inst_in,

    addr => pc_out,
    inst_out => inst
);
```

Stage 2

--Stage 2: Decode and Read Operands

```
RF_inst: RF port map (  
    CLK => CLK,  
    rst => RESET,  
  
    write_En => rf_we,  
    index => rf_loadindex,  
    data => rf_datain,  
    wr_reg => rf_wr_reg,  
    rd_reg1 => inst_IFID(9 downto 5),  
    rd_reg2 => inst_IFID(14 downto 10),  
    rd_reg3 => inst_IFID(19 downto 15),  
    rs1 => rs1,  
    rs2 => rs2,  
    rs3 => rs3  
);
```

Stage 3

--Stage 3:Execute

```
ControlUnit_EX: ControlUnit  
port map(  
    inst => inst_IDEX,  
  
    control => control,  
    write_en => open,  
    immediate => immediate,  
    loadIndex => loadIndex  
);
```

Stage 4

```
--stage 4: Write back
--control
ControlUnit_WB: ControlUnit
port map(
    inst => inst_EXWB,


    control => open,
    write_en => rf_we,
    immediate => open,
    loadIndex => rf_loadIndex
);
rf_datain <= alu_out_EXWB;
rf_wr_reg <= inst_EXWB(4 downto 0);

DataForwarding_inst: DataForwarding
port map(
    rf_we => rf_we,
    rf_wr_reg => rf_wr_reg,

    rs1_reg => inst_IDEX(9 downto 5),
    rs2_reg => inst_IDEX(14 downto 10),
    rs3_reg => inst_IDEX(19 downto 15),


    fw1 => fw1,
    fw2 => fw2,
    fw3 => fw3
);
```

Pipeline Output

 


Assembler

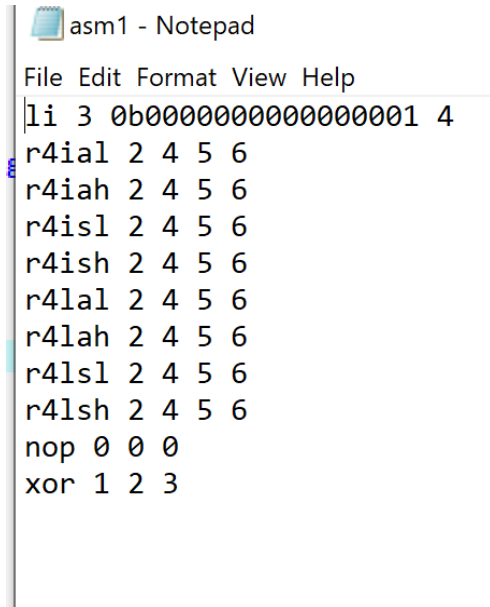The assembler was a separate program. It converts an assembly file to the binary format for the instruction buffer.



```
asm1 - Notepad
File Edit Format View Help
li 3 0b0000000000000001 4
r4ial 2 4 5 6
r4iah 2 4 5 6
r4isl 2 4 5 6
r4ish 2 4 5 6
r4lal 2 4 5 6
r4lah 2 4 5 6
r4lsl 2 4 5 6
r4lsh 2 4 5 6
nop 0 0 0
xor 1 2 3
```

Output for Assembler

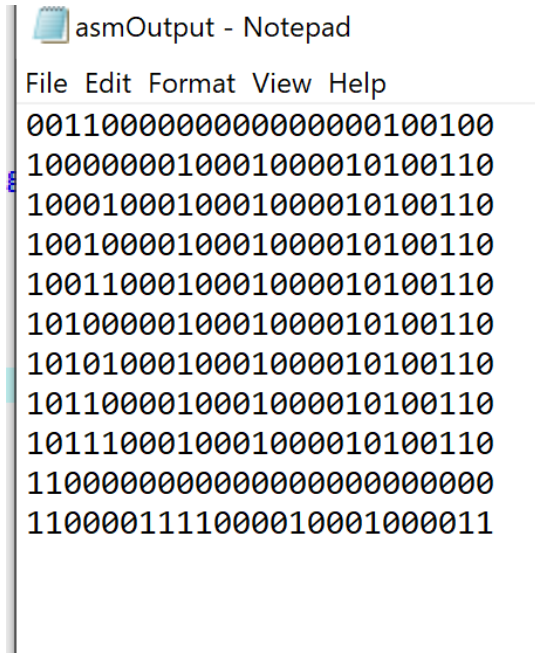

```
asmOutput - Notepad
File Edit Format View Help
0011000000000000000100100
1000000010001000010100110
1000100010001000010100110
1001000010001000010100110
1001100010001000010100110
1010000010001000010100110
1010100010001000010100110
1011000010001000010100110
1011100010001000010100110
110000000000000000000000
1100001111000010001000011
```

Conclusion:

The finished product of the pipeline was successful in properly pushing data through and handling multiple instructions at once. The individual units and registers in the pipeline are properly functioning as shown above in the simulations. The pipeline contained core units such as the Instruction Buffer, Register File, and the ALU. Interstate registers carried data to each unit to be processed, where it was then passed onto the next register. The goal of the pipeline was to allow all major units to be busy at all times by acting as an assembly line. Multiple instructions are able to be processed by splitting the workload and simply moving the data through the pipeline. The block diagram illustrates how the pipeline should act with data transfer. The only part I wasn't able to accomplish was to have a results file that highlights all the important signals for all stages of the pipeline, for all cycles of execution.